



# Welcome to LAB Protocol





# VNR VJIET – VNR LAB Protocol

## Power Electronics and Simulation Laboratory

Mr. B.Ganesh babu

Dr.J.Srinivasa Rao

Mr.G.Laxmi Narayana




# Power Electronics

- ✓ Power electronics is the technology associated with the efficient conversion, control and conditioning of electric power by static means from its available input form into desired electrical output form.
- ✓ The goal of power electronics is to control the flow of energy from an electrical source to an electrical load with high efficiency, high availability, high reliability, small size, light weight and low cost.
- ✓ The Power conversion systems according to the type of the input and output power are :
  - AC to DC Conversion
  - DC to AC Conversion
  - DC to DC Conversion
  - AC to AC Conversion




# The Interdisciplinary Nature

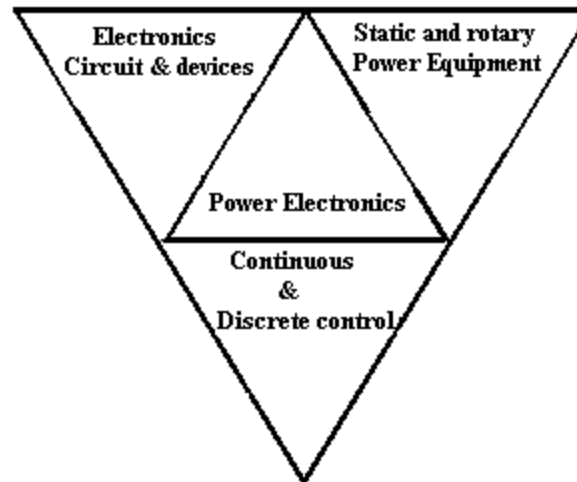



## Relation with multiple disciplines

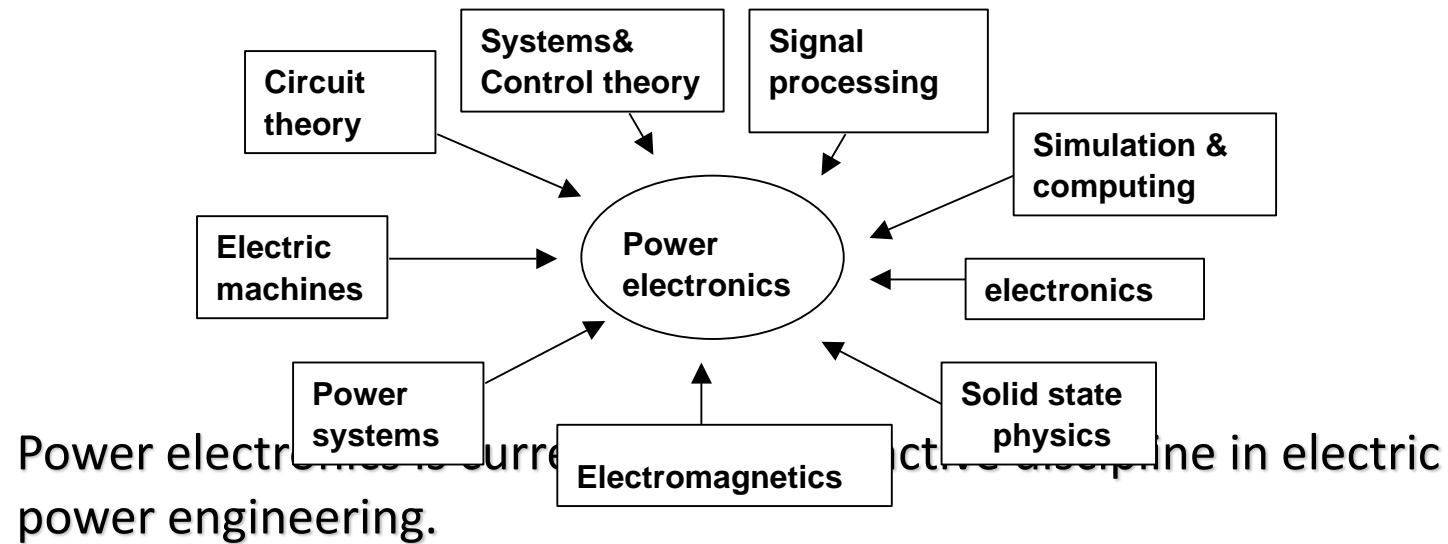

# Classification of Power Electronic Devices


The following is taken from Principles and Applications of Electrical Engineering by G. Rizzoni, McGraw Hill

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Device	Device symbol
Diode	
Thyristor	
Gate turnoff thyristor (GTO)	
Triac	
<i>npn</i> BJT	
IGBT	
<i>n</i> -channel MOSFET	



# The Evolution of Power electronics

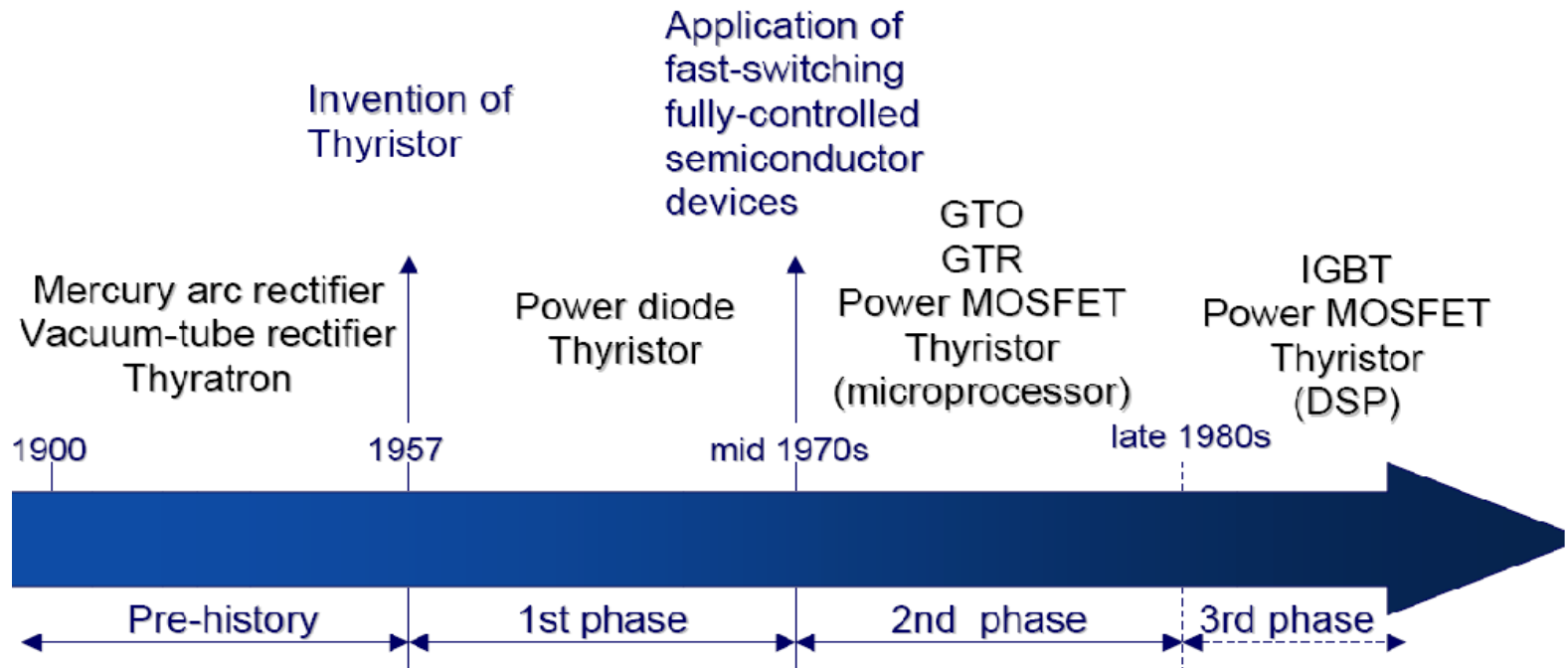

The power electronics revolution has gained momentum since the late 1980s



# Power Electronic Devices



Vacuum tube



Thyratron






## The Evolution of Power electronics



Thyristor (SCR), GTO, Triac

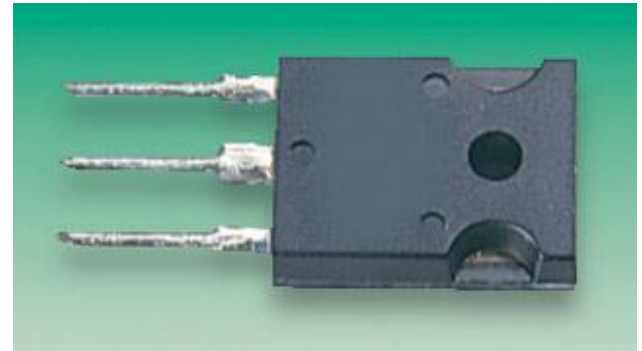

Power MOSFET, IGBT



## Comparison between different commonly used Thyristors

- ✍ Line Commutated Thyristors available up to 6000V, 4500A.
- ✍ Ex: Converter grade (line commutated) SCR.
- ✍ V / I rating: 5KV / 5000A
- ✍ Max. Frequency: 60Hz.
- ✍ Switching time: 100 to 400 $\mu$ sec.
- ✍ On state resistance: 0.45m $\Omega$ .
  
- ✍ Example of Inverter Grade Thyristor Ratings
- ✍ V / I rating: 4500V / 3000A.
- ✍ Max. Frequency: 20KHz.
- ✍ Switching time: 20 to 100 $\mu$ sec.
- ✍ On state resistance: 0.5m $\Omega$ .



## Ratings of MOSFET & IGBT

- ✍ MOSFET V / I rating 700V, 3.3A.
- ✍ Max. Frequency: Over 500kHz.
- ✍ Switching time around ( $T_{on}$ )  $1\mu\text{sec}$ .
- ✍ On state resistance:  $3.6\Omega$ .
  
- ✍ IGBT V / I rating 1200V, 3A.
- ✍ Max. Frequency: Over 500kHz.
- ✍ Switching time around ( $T_{on}$ )  $1.2\mu\text{sec}$ .
- ✍ On state resistance:  $1.78\Omega$ .

# Power Electric Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


Circuit type	Essential features
Voltage regulators	Regulate a DC supply to a fixed voltage output
Power amplifiers	Large-signal amplification of voltages and currents
Switches	Electronic switches (e.g., transistor switches)
Diode rectifier	Converts fixed AC voltage (single- or multiphase) to fixed DC voltage
AC-DC converter (controlled rectifier)	Converts fixed AC voltage (single- or multiphase) to variable DC voltage
AC-AC converter (AC voltage controller)	Converts fixed AC voltage to variable AC voltage (single- or multiphase)
DC-DC converter (chopper)	Converts fixed DC voltage to variable DC voltage
DC-AC converter (inverter)	Converts fixed DC voltage to variable AC voltage (single- or multiphase)

## Scope of Power Electronics

<i>Power Level (Watts)</i>	<i>System</i>
0.1-10	<ul style="list-style-type: none"> <li>• Battery-operated equipment</li> <li>• Flashes/strobes</li> </ul>
10-100	<ul style="list-style-type: none"> <li>• Satellite power systems</li> <li>• Typical offline flyback supply</li> </ul>
100 – 1kW	<ul style="list-style-type: none"> <li>• Computer power supply</li> <li>• Blender</li> </ul>
1 – 10 kW	<ul style="list-style-type: none"> <li>• Hot tub</li> </ul>
10 – 100 kW	<ul style="list-style-type: none"> <li>• Electric car</li> <li>• Eddy current braking</li> </ul>
100 kW –1 MW	<ul style="list-style-type: none"> <li>• Bus</li> <li>• micro-SMES</li> </ul>
1 MW – 10 MW	<ul style="list-style-type: none"> <li>• SMES</li> </ul>
10 MW – 100 MW	<ul style="list-style-type: none"> <li>• Magnetic aircraft launch</li> <li>• Big locomotives</li> </ul>
100 MW – 1 GW	<ul style="list-style-type: none"> <li>• Power plant</li> </ul>
> 1 GW	<ul style="list-style-type: none"> <li>• Sandy Pond substation (2.2 GW)</li> </ul>
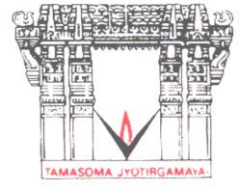
# Applications


- ✓ Commercial: Air Conditioners, Central Refrigeration, [UPS](#), Elevators, Emergency Lamps, Heating Systems.
- ✓ Domestic: Cooking Equipments, Lightning & heating systems, [Air conditioners](#), Refrigerators, Freezers, Personal Computers, [washing machines](#).
- ✓ Telecommunications: Mobile Battery Chargers, Modular DC Supplies .
- ✓ Transportation: [Electric vehicles](#), MAGLEV Trains, Battery operated vehicles, ship power systems, Air craft power system, Trains & locomotives.
- ✓ Industrial: Motor drives, Electrolysis, Induction heating, Welding, Arc furnaces, ovens.



# Applications


- ✓ Utility Systems: HVDC, FACTS devices like TCR, TCSC, STATCOM, UPFC, UPQC, Power Quality Control, Reactive power compensation .
- ✓ Renewable Energy Sources: Variable Speed Technology, Active and reactive power control, power conditioning.
- ✓ Military & Aerospace: Unmanned Aerial Vehicles, Unmanned ground vehicles, manned aircraft & spacecraft.

# Inverter Controlled Air Conditioners

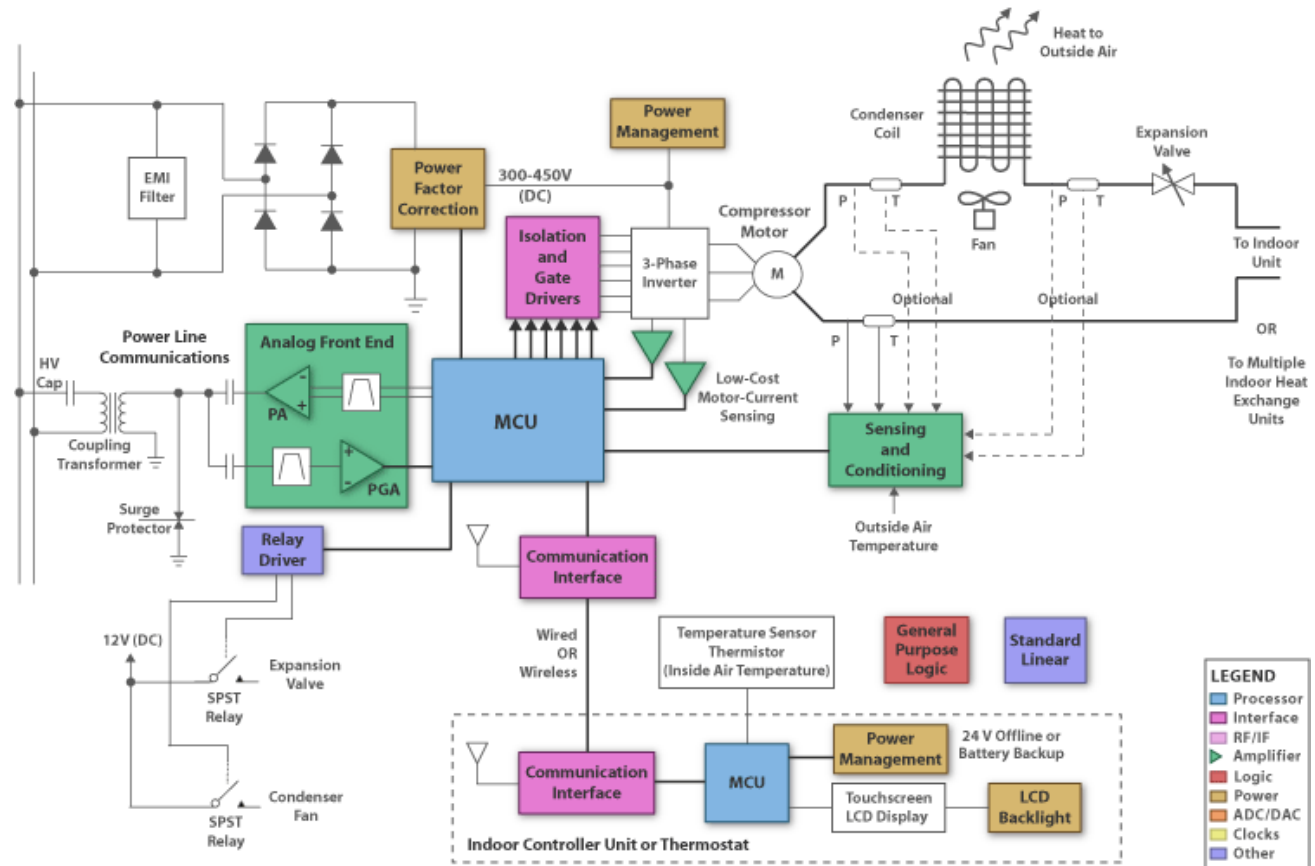





# Inverter Controlled Washing Machine

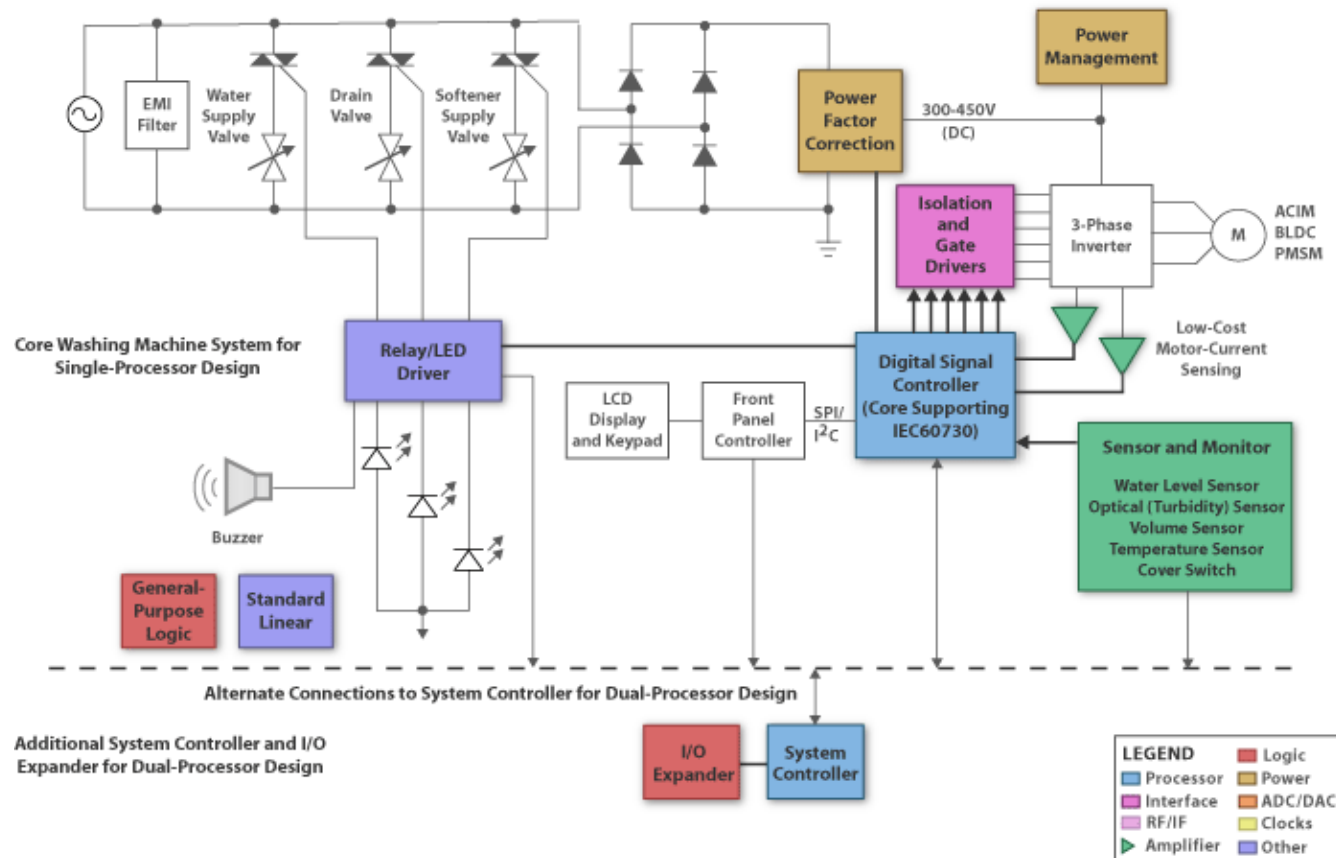

# Uninterruptible Power Supply

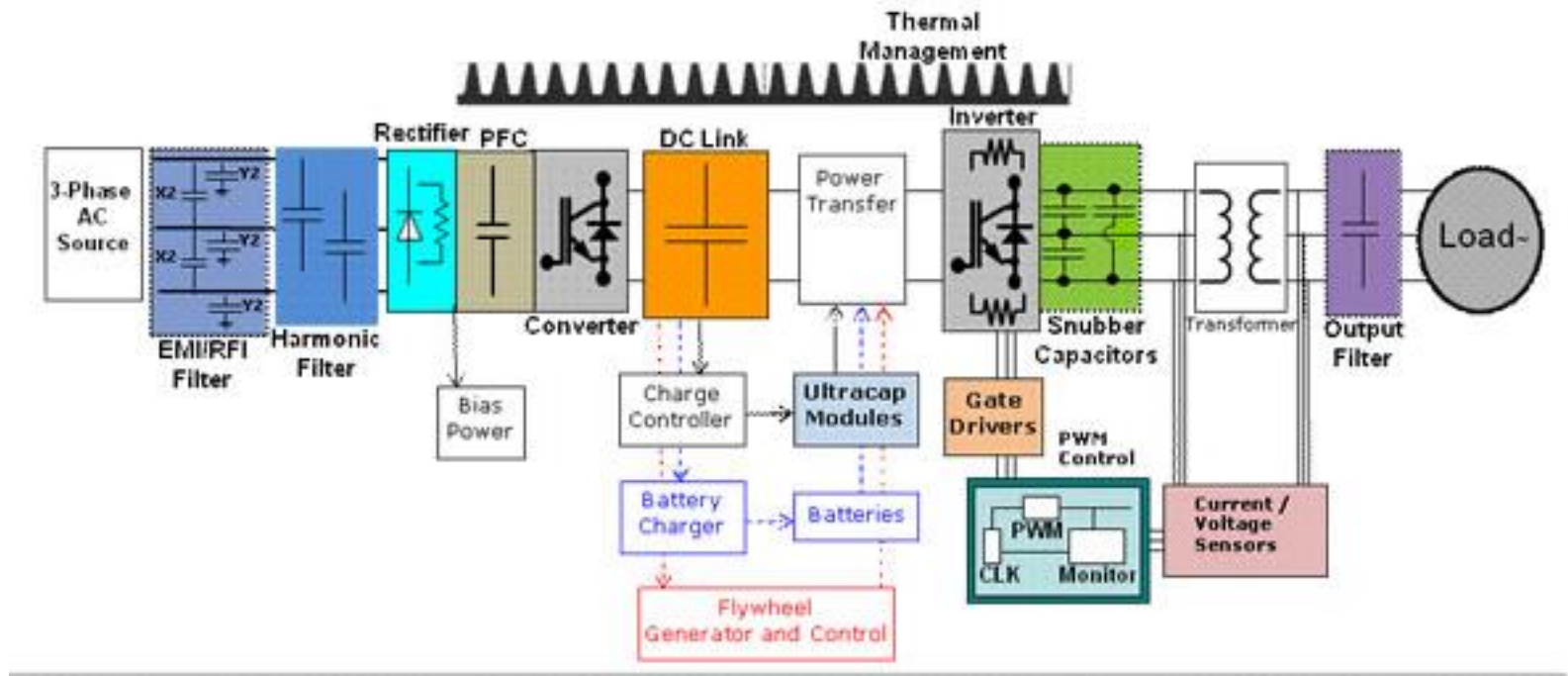


# Hybrid Vehicle

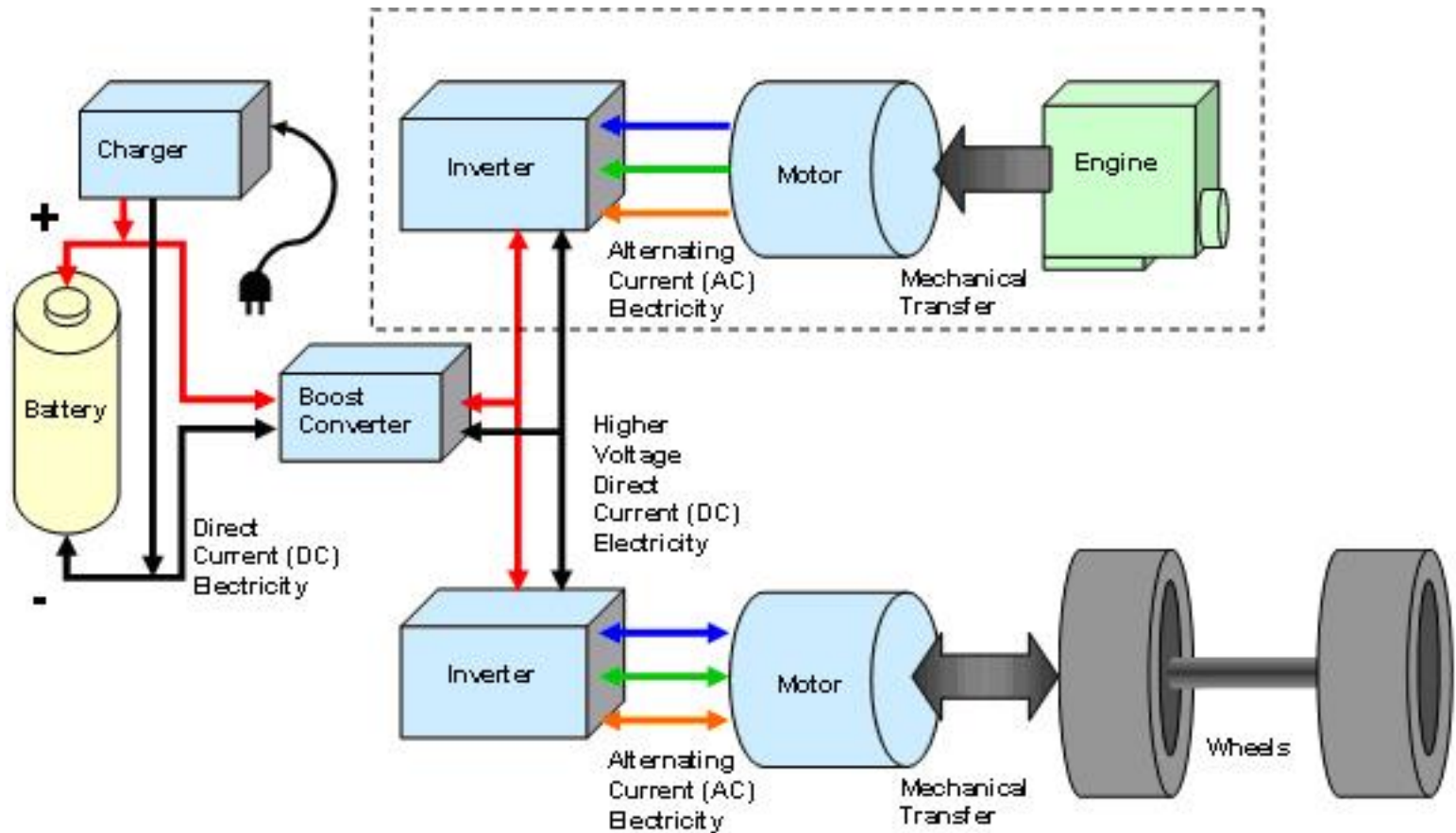


# Renewable energy sources

## Photovoltaics

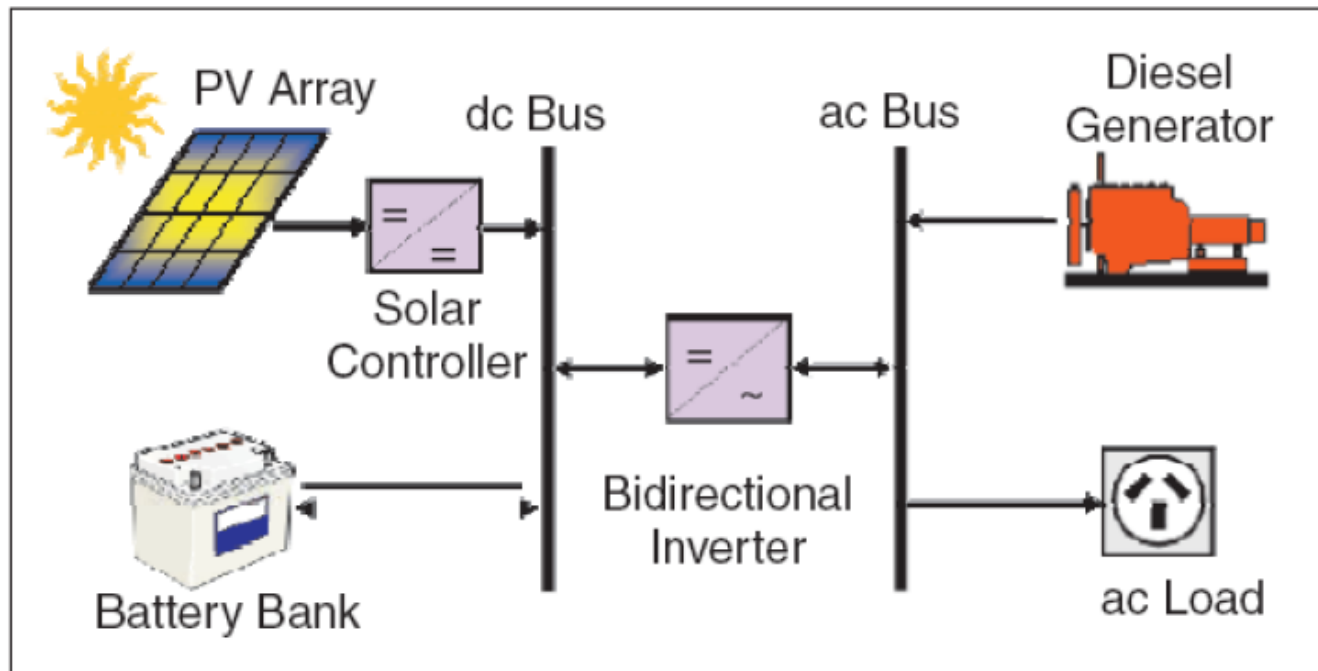



# Applications of Power Devices

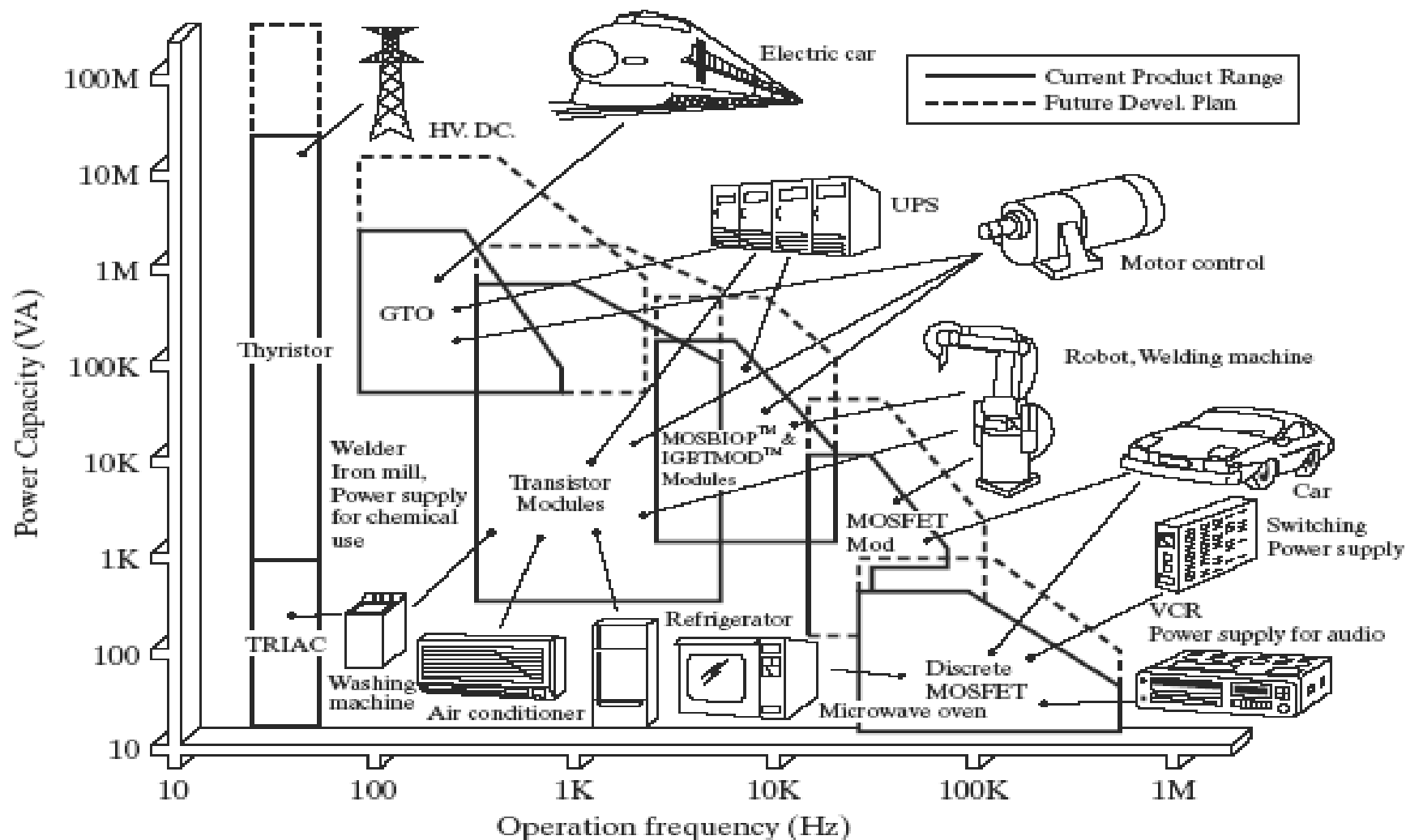



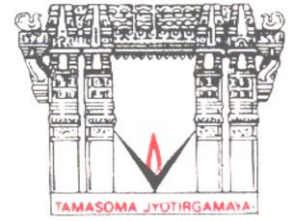
## **FPGAs and Plug-in Hybrid Vehicles** **Power Electronics, FPGA, Applications**

- **FPGAs and Plug-in Hybrid Vehicles**
- **Sep.15, 2010 in**  
**Motor Control IP,**  
**Technology, Power**  
**Electronics, FPGA,**  
**Applications**





# ***Electrical Circuits and Simulation Lab***

***Part A :*** HARDWARE EXPERIMENTS

***Part B :*** ***SIMULATION***

# PART A





1. Study of Characteristics of SCR, MOSFET & IGBT
2. Study of UJT gate firing circuit for SCR
3. Single Phase AC Voltage Controller with R and RL Loads
4. Single Phase fully controlled bridge converter with R and RL loads
- 5 Single Phase Cyclo-converter with R and RL loads
6. Single Phase half controlled converter with R load
7. Three Phase half controlled bridge converter with R-load
8. Single Phase Bridge inverter with R and RL loads
9. Study of buck converter
10. Study of boost converter



**PART-B**

1. (a) Simulation of single-phase Half wave converter using R and RL loads  
(b) Simulation of single-phase full converter using R, RL and RLE loads  
(c) Simulation of single-phase Semi converter using R, RL and RLE loads
2. (a) Simulation of Single-phase AC voltage controller using R and RL loads  
(b) Simulation of Single phase Cyclo-converter with R and RL-loads
3. Simulation of Buck chopper
4. Simulation of single phase Inverter with PWM control.
5. Simulation of three phase fully controlled converter with R and RL loads, with and without freewheeling diode. Observation of waveforms for Continuous and Discontinuous modes of operation.
6. Study of PWM technique

# Single Phase Half Controlled Converter

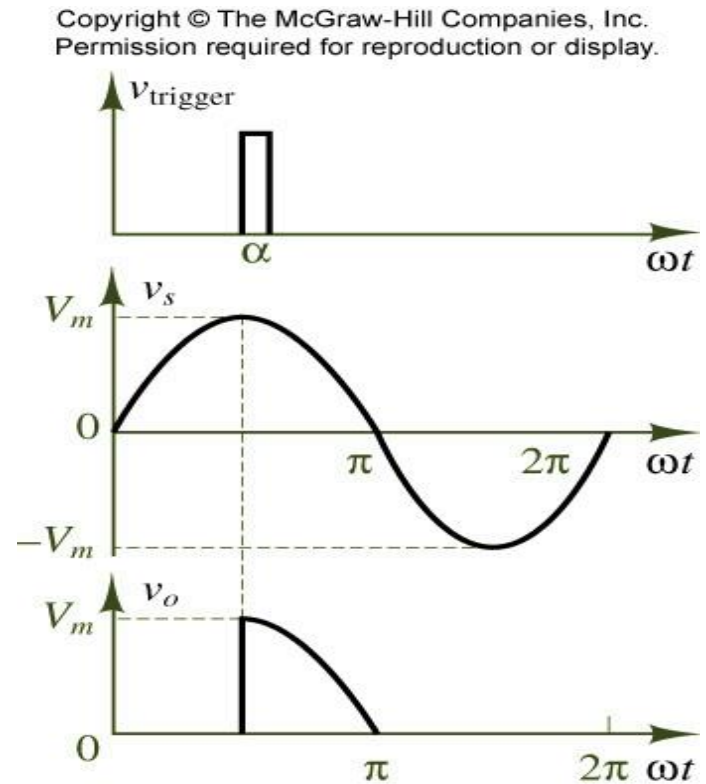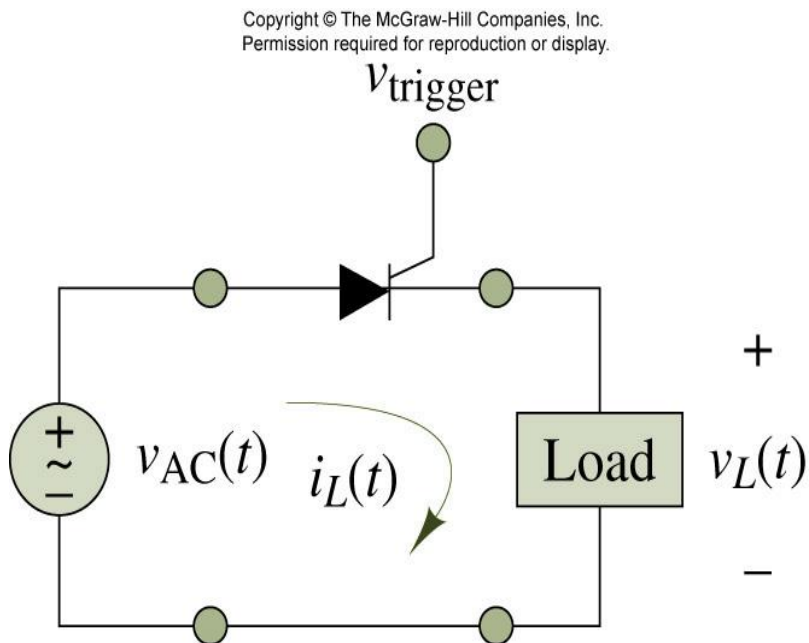
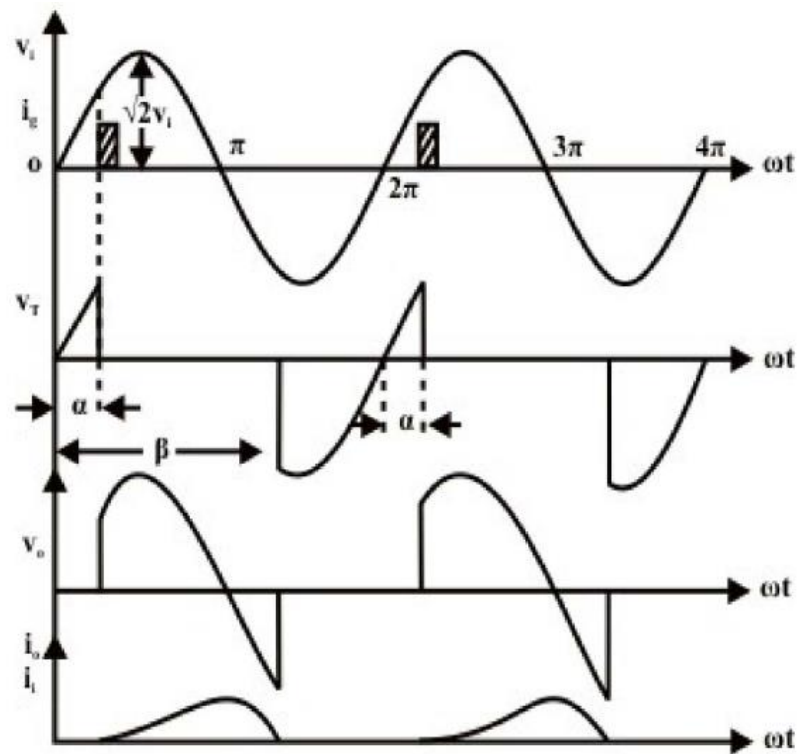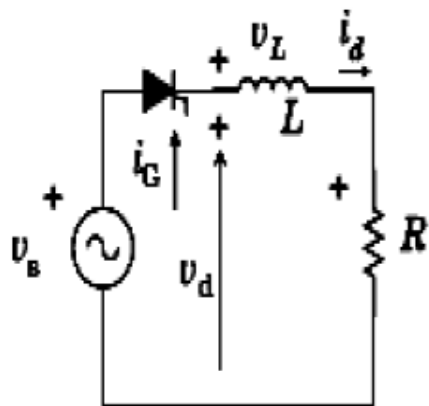
## Single Phase Half Controlled Converter with RL-Load





## Circuit Operation

---


- ✓ At  $\omega t = 0$  when the input supply voltage becomes positive the thyristor T becomes forward biased. However, unlike a diode, it does not turn ON till a gate pulse is applied at  $\omega t = \alpha$ . During the period  $0 < \omega t \leq \alpha$ , the thyristor blocks the supply voltage and the load voltage remains zero as shown.
- ✓ Consequently, no load current flows during this interval.
- ✓ As soon as a gate pulse is applied to the thyristor at  $\omega t = \alpha$  it turns ON. The voltage across the thyristor collapses to almost zero and the full supply voltage appears across the load. From this point onwards the load voltage follows the supply voltage. The load being purely resistive the load current  $i_o$  is proportional to the load voltage.


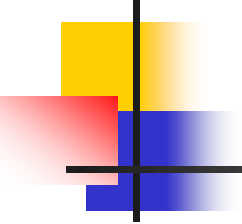
## Circuit Operation

---

- ✓ At  $\omega t = \pi$  as the supply voltage passes through the negative going zero crossing the load voltage and hence the load current becomes zero and tries to reverse direction. In the process the thyristor undergoes reverse recovery and starts blocking the negative supply voltage.
- ✓ Therefore, the load voltage and the load current remains clamped at zero till the thyristor is fired again at  $\omega t = 2\pi + \alpha$ . The same process repeats there after.



---

From above discussion one can write.

For  $\alpha \leq \omega t \leq \beta$

$$v_0 = v_i = \sqrt{2} V_i \sin \omega t$$

$v_0 = 0$  otherwise

Therefore

$$\begin{aligned} V_{OAV} &= \frac{1}{2\pi} \int_0^{2\pi} v_0 d\omega t \\ &= \frac{1}{2\pi} \int_{\alpha}^{\beta} \sqrt{2} V_i \sin \omega t d\omega t \\ &= \frac{V_i}{\sqrt{2}\pi} (\cos \alpha - \cos \beta) \end{aligned}$$

$$\begin{aligned} V_{ORMS} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_0^2 d\omega t} \\ &= \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} 2V_i^2 \sin^2 \omega t d\omega t} \\ &= \frac{V_i}{\sqrt{2}} \left( \frac{\beta - \alpha}{\pi} + \frac{\sin 2\alpha - \sin 2\beta}{2\pi} \right)^{\frac{1}{2}} \end{aligned}$$

$$I_{OAV} = \frac{V_{OAV}}{R} = \frac{V_i}{\sqrt{2}\pi R} (\cos \alpha - \cos \beta)$$





## Applications of Half Controlled Converter

---

- ✍ Electric Welding.
- ✍ Electroplating of metals.
- ✍ Electrorefining of metals.
- ✍ Motor speed control.

- Commutation
- Thyristor voltages and currents
- Transformer current

$$U_d = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} U_2 \sin \omega t d(\omega t) = \frac{2\sqrt{2}}{\pi} U_2 \cos \alpha = 0.9 U_2 \cos \alpha$$

$$I_{dVT} = \frac{1}{2} I_d \quad I_{VT} = \frac{1}{\sqrt{2}} I_d$$



$$I_2 = I_d$$

$$0 \leq \alpha \leq \frac{\pi}{2}$$

$$\theta = 180^\circ$$

$$U_{DM} = U_{RM} = \sqrt{2} U_2$$
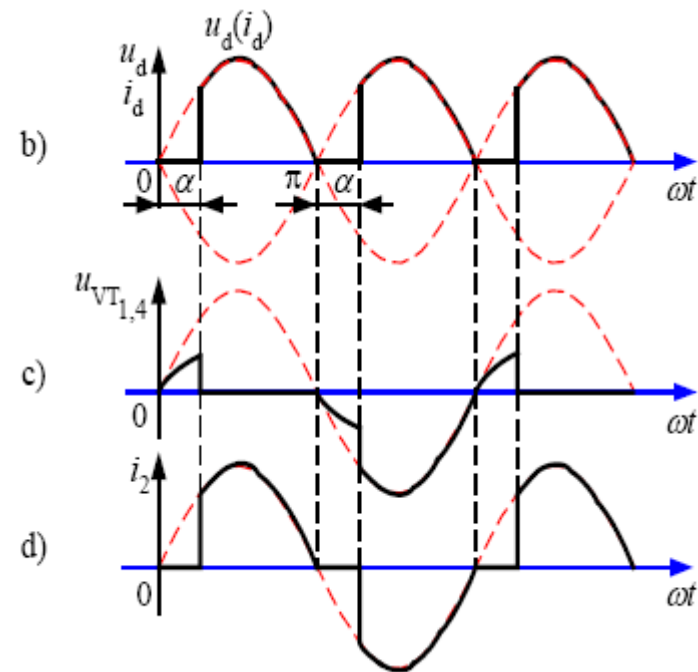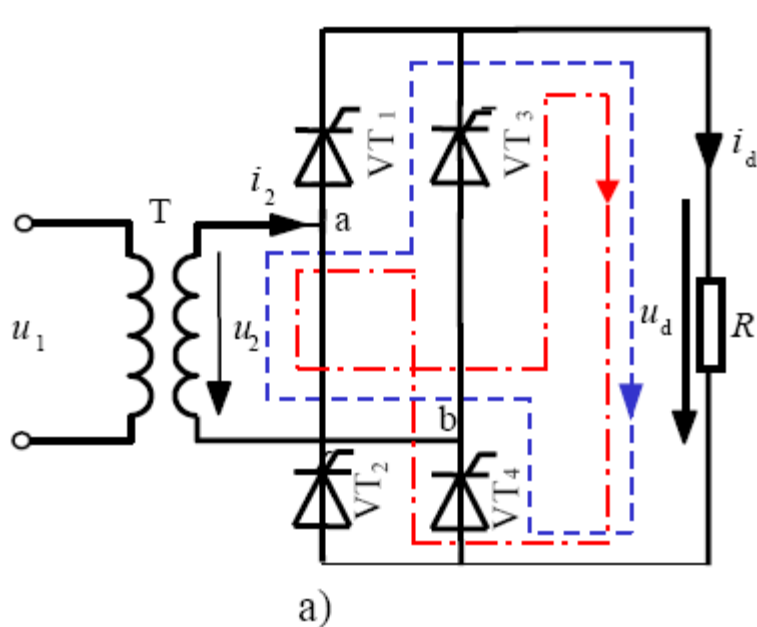
# Single Phase Fully controlled bridge converter with R load.



➤ Assumption:  $L_s=0$

For thyristor: maximum forward voltage, maximum reverse voltage

Advantages: — 2 pulses in one line cycle

— No DC component in the transformer current

- Average output (rectified) voltage

$$U_d = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2} U_2 \sin \omega t d(\omega t) = \frac{2\sqrt{2} U_2}{\pi} \frac{1 + \cos \alpha}{2} = 0.9 U_2 \frac{1 + \cos \alpha}{2}$$

- **Average output current**

$$I_d = \frac{U_d}{R} = \frac{2\sqrt{2} U_2}{\pi R} \frac{1 + \cos \alpha}{2} = 0.9 \frac{U_2}{R} \frac{1 + \cos \alpha}{2}$$

$$I_{dVT} = \frac{1}{2} I_d = 0.45 \frac{U_2}{R} \frac{1 + \cos \alpha}{2}$$



- **For thyristor**

$$I_{VT} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \left( \frac{\sqrt{2} U_2}{R} \sin \omega t \right)^2 d(\omega t)} = \frac{U_2}{\sqrt{2} R} \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}}$$

- **For transformer**  $I = I_2 = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} \left( \frac{\sqrt{2} U_2}{R} \sin \omega t \right)^2 d(\omega t)} = \frac{U_2}{R} \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}}$

$$0 \leq \alpha \leq \pi$$
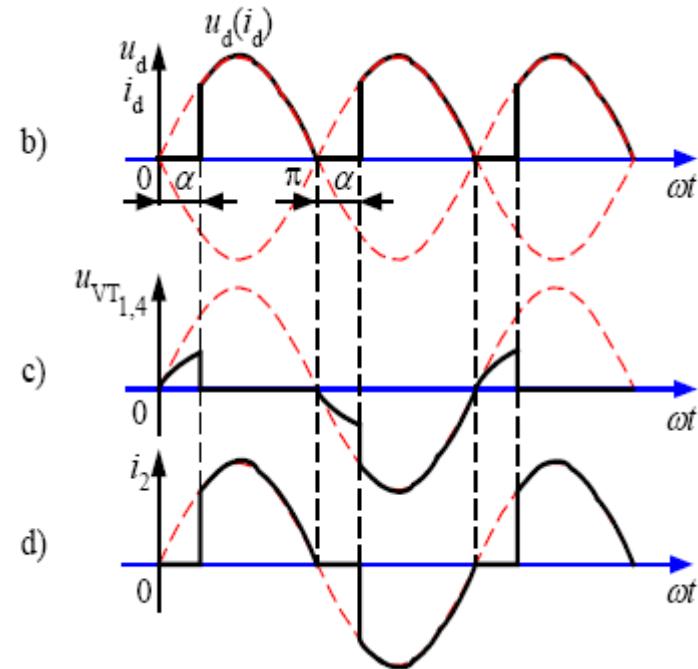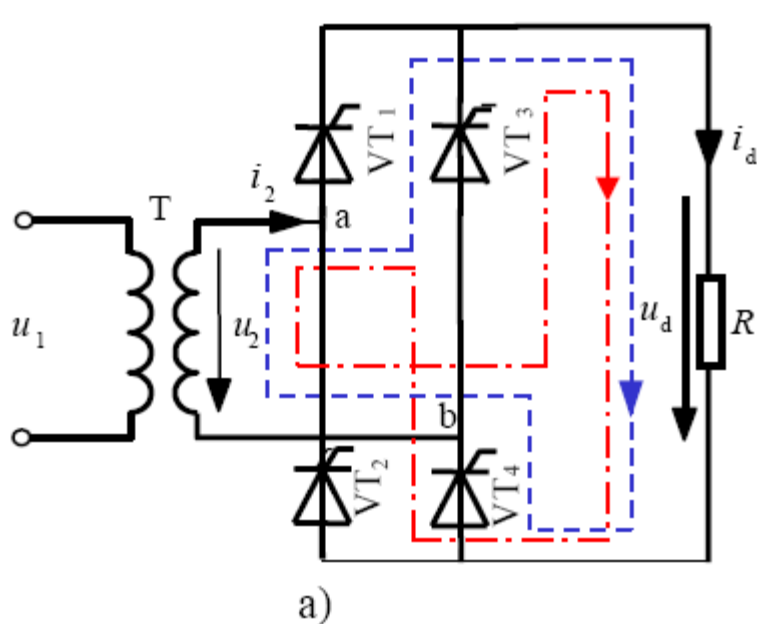
# Single Phase Fully controlled bridge converter with R load.



➤ Assumption:  $L_s=0$

For thyristor: maximum forward voltage, maximum reverse voltage

Advantages: — 2 pulses in one line cycle  
— No DC component in the transformer current

- Commutation
- Thyristor voltages and currents
- Transformer current

$$U_d = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} U_2 \sin \omega t d(\omega t) = \frac{2\sqrt{2}}{\pi} U_2 \cos \alpha = 0.9 U_2 \cos \alpha$$

$$I_{dVT} = \frac{1}{2} I_d \qquad I_{VT} = \frac{1}{\sqrt{2}} I_d$$

$$I_2 = I_d$$

$$0 \leq \alpha \leq \frac{\pi}{2}$$


$$\theta = 180^\circ$$

$$U_{DM} = U_{RM} = \sqrt{2} U_2$$




An AC to DC converter circuit can convert AC voltage into a DC voltage. The DC output voltage can be controlled by varying the firing angle of the thyristors. The AC input voltage could be a single phase or three phase.
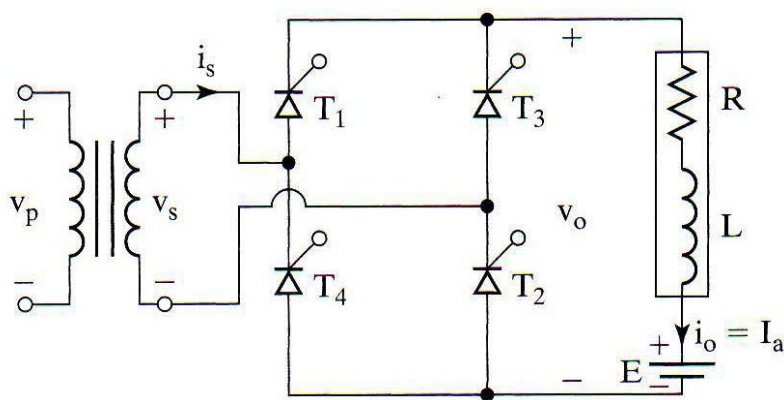
## Single phase, Full wave AC to DC converter



(a) Circuit

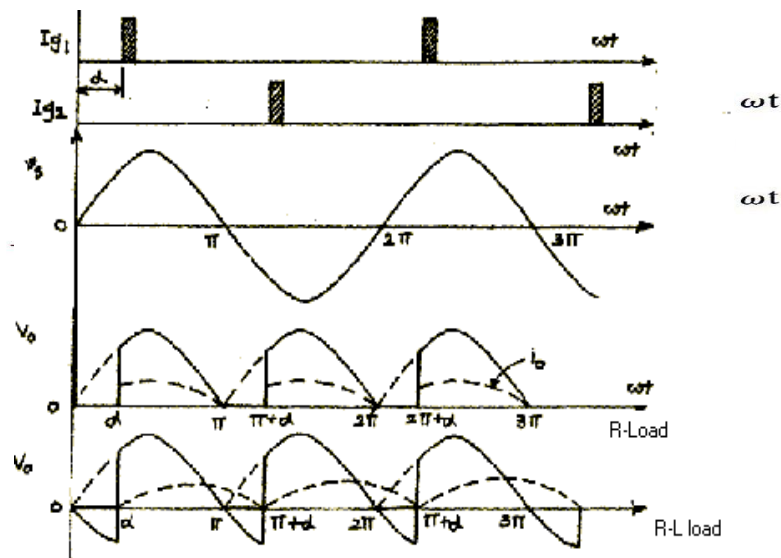

The average output voltage can be found from

:

$$V_{dc} = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t) = \frac{2V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi+\alpha}$$

$$= \frac{2V_m}{\pi} \cos \alpha$$

➤ Assumption:

$\alpha = 0^\circ$  and  $L_s = 0$ , so

$$\frac{U_d}{U_{d0}} = \cos \alpha \quad U_{d0} = \frac{1}{\pi} \int_0^\pi \sqrt{2} U_2 \cdot \sin \omega t \cdot d(\omega t) = \frac{2\sqrt{2}}{\pi} U_2 = 0.9 U_2$$

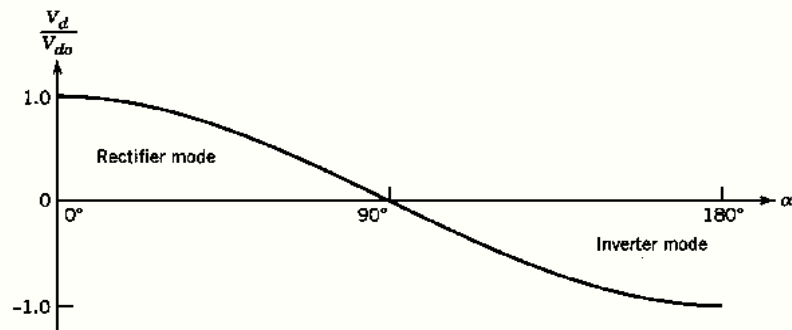


Figure 6-7 Normalized  $V_d$  as a function of  $\alpha$ .


- Rectifier mode
- Inverter mode

➤ Average Power:

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T u_d i_d dt = I_d \left( \frac{1}{T} \int_0^T u_d dt \right) = I_d U_d = 0.9 U_2 I_d \cos \alpha$$





# 3-phase full wave converter

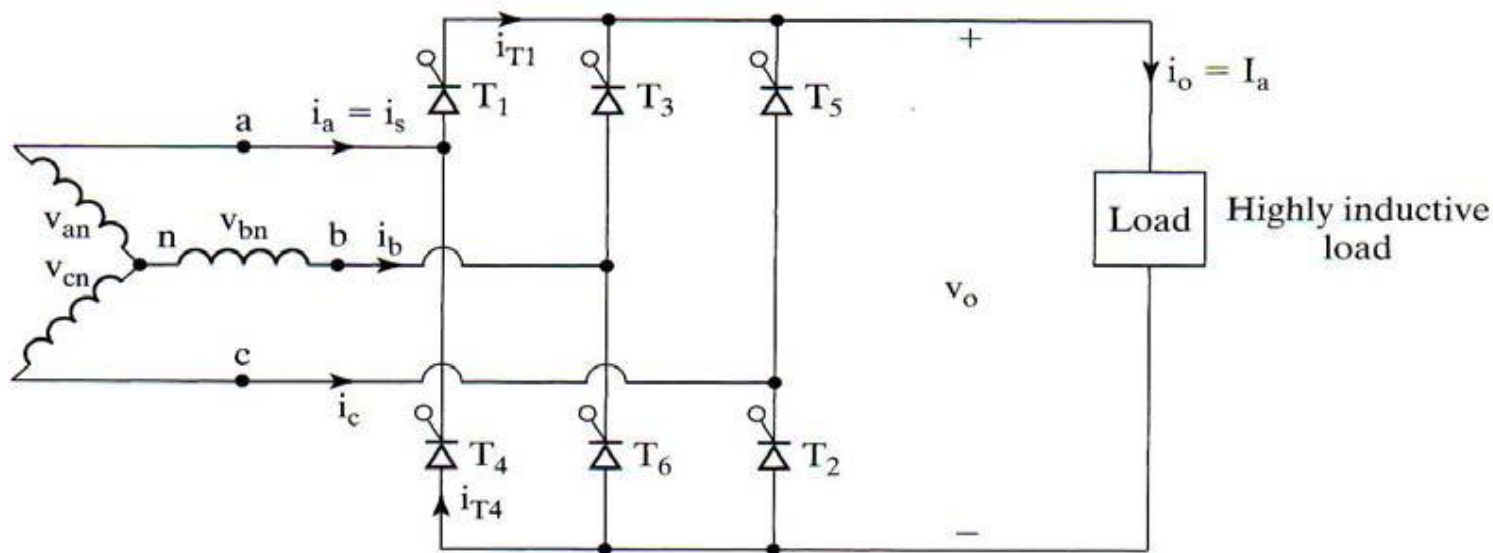

(a) Circuit

# 1-phase cycloconverter

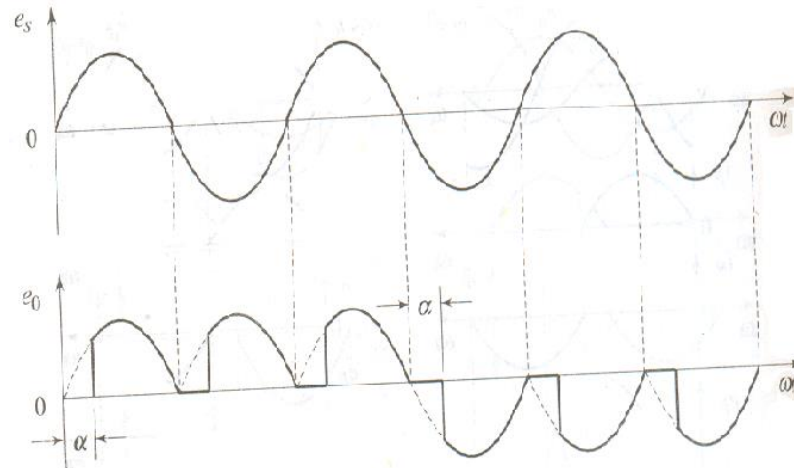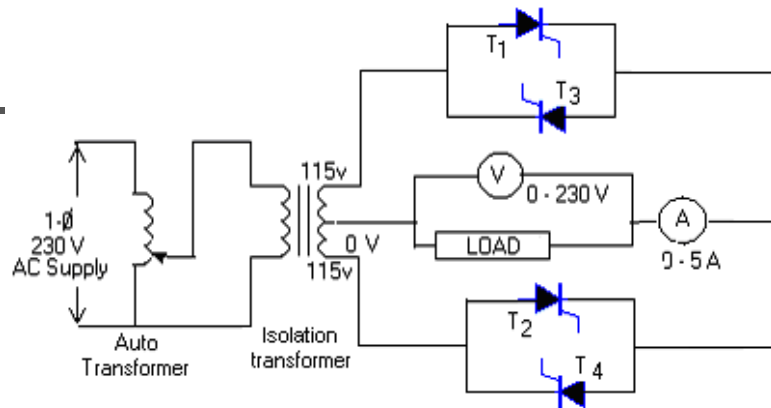

# AC- Voltage controller with R -Load

